
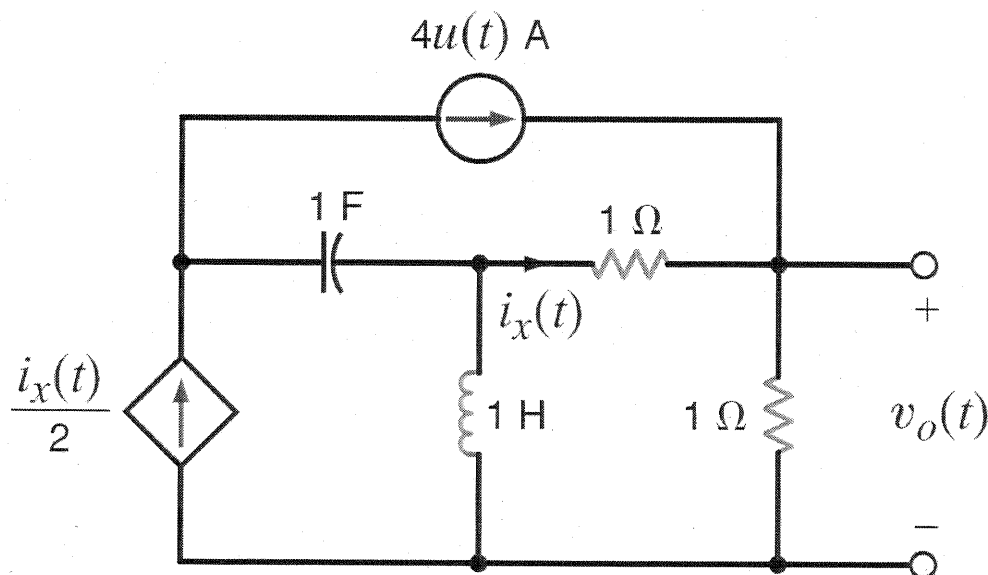


**14.16** Use mesh analysis to find  $v_o(t)$ ,  $t > 0$ , in the network in Fig. P14.16. **CS**

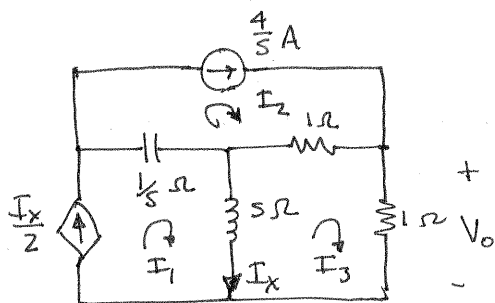

**Figure P14.16**

**SOLUTION:**



$$I_1 = I_x = \frac{I_1 - I_3}{2} \Rightarrow I_1 = -I_3$$

$$I_2 = 4/s$$

$$I_3(s+2) - sI_1 - I_2 = 0$$

$$V_o = (1)I_3$$

$$I_3(s+2) + sI_3 = 4/s \Rightarrow I_3 = \frac{4}{s(2s+2)} = \frac{2}{s(s+1)}$$

$$V_o = \frac{2}{s(s+1)} = \frac{2}{s} - \frac{2}{s+1}$$

$$v_o(t) = [2(1 - e^{-t})]u(t)$$