
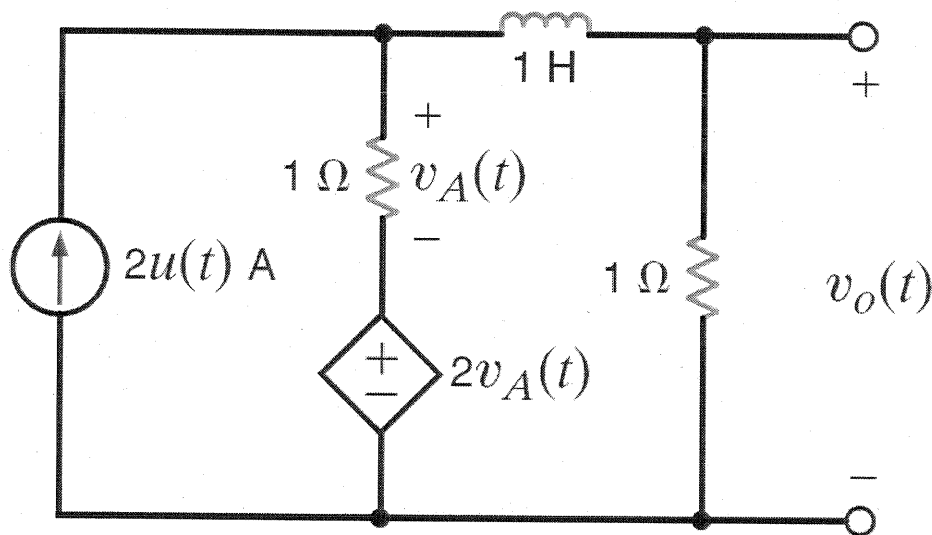


**14.25** Use Thévenin's theorem to find  $v_o(t)$ ,  $t > 0$ , in the network shown in Fig. P14.25. **PSV**

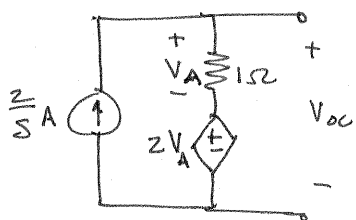


**Figure P14.25**

**SOLUTION:**



$$V_{OC} = 3V_A \quad \& \quad V_A = (1)(2/s)$$


$$V_{OC} = 6/s$$

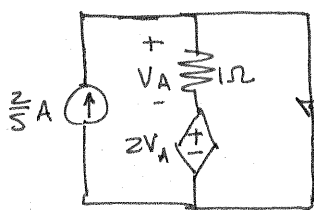

$$I_{SC} = \frac{2}{s}$$

$$Z_{TH} = V_{OC} / I_{SC}$$

$$Z_{TH} = 3\Omega$$

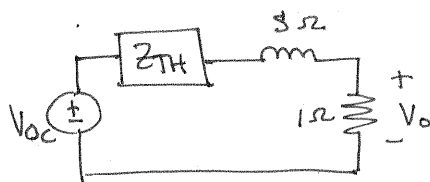

$$v_o = \frac{V_{OC}(1)}{s+1+Z_{TH}} = \frac{6}{s(s+4)} = \frac{3/2}{s} - \frac{3/2}{s+4}$$

$$v_o(t) = [1.5(1 - e^{-4t})]u(t) \text{ V}$$