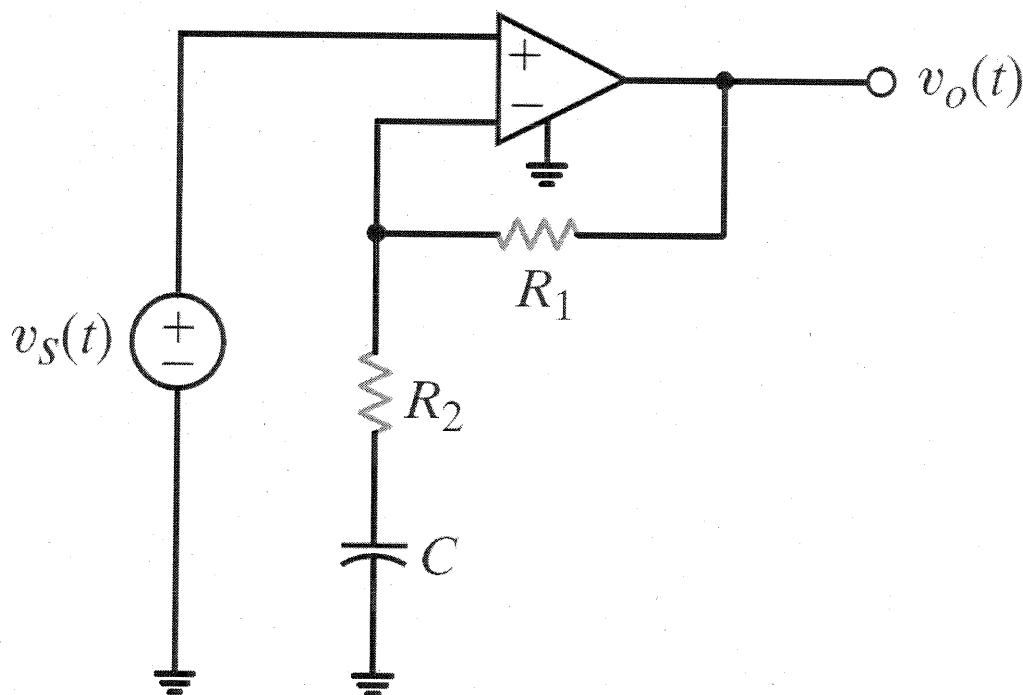


**14.47** Find the transfer function for the network shown in Fig. P14.47.



**Figure P14.47**

**SOLUTION:** Let  $z_2 = R_1$  &  $z_1 = R_2 + \frac{1}{sC} = \frac{R_2Cs + 1}{sC}$

$$\frac{V_o}{V_s} = 1 + \frac{z_2}{z_1} = 1 + \frac{R_1Cs}{R_2Cs + 1} = \frac{(R_1 + R_2)Cs + 1}{R_2Cs + 1}$$

$$\boxed{\frac{V_o}{V_s} = \left(1 + \frac{R_1}{R_2}\right) \left(\frac{s + \frac{1}{CR_2}}{s + \frac{1}{CR_2}}\right) \quad R = R_1 + R_2}$$