

14.60 Determine the steady-state response $i_o(t)$ for the network in Fig. P14.60.


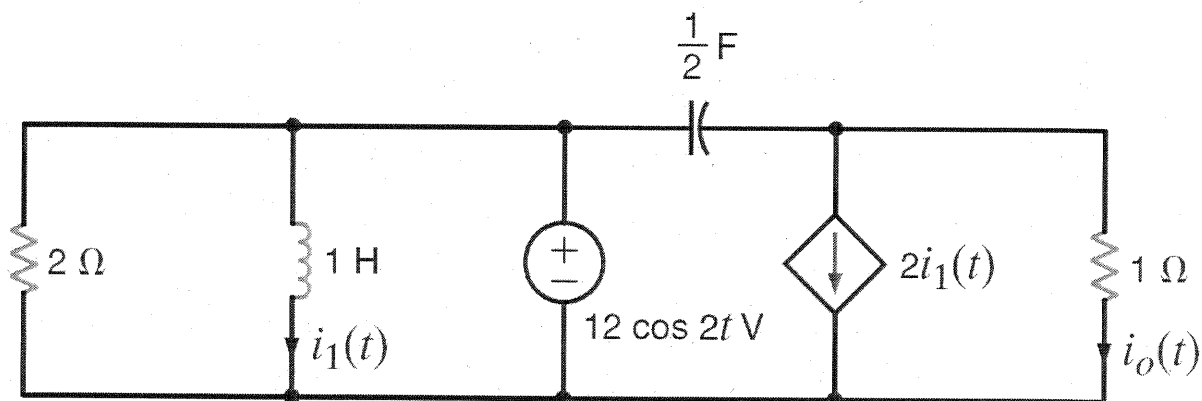


Figure P14.60

SOLUTION: Use KCL,

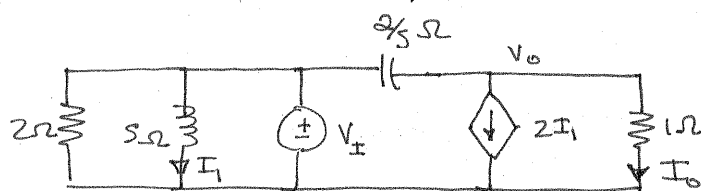

$$I_1 = \frac{V_1}{s}$$

$$I_o = \frac{V_o}{1}$$

$$\frac{V_o - V_1}{2/s} + 2I_1 + \frac{V_o}{1} = 0 \Rightarrow V_o \left(\frac{s}{2} + 1 \right) = V_1 \left(\frac{s}{2} - \frac{2}{s} \right)$$

$$\frac{V_o}{V_1} = \frac{s-2}{s} \Rightarrow I_o = \frac{V_1(s-2)}{s}$$

At steady-state, $V_1 = 12 \angle 0^\circ \text{ V}$ & $s = j2$

$$I_o = 12\sqrt{2} \angle 45^\circ \text{ A}$$

$$i_o(t) = 12\sqrt{2} \cos(2t + 45^\circ) \text{ A}$$