

14.61 Find the steady-state response $i_o(t)$ for the network shown in Fig. P14.61. **CS**


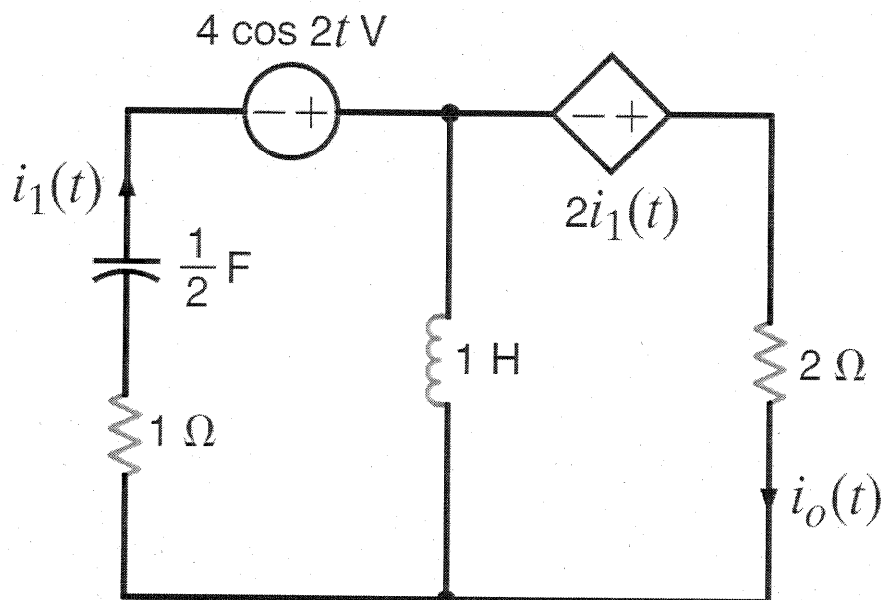


Figure P14.61

SOLUTION:

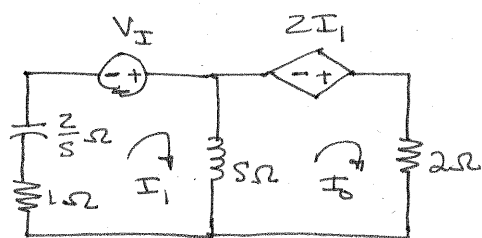

$$V_I = I_1(s + 1 + 2/s) - sI_0$$

$$= I_1 \left(\frac{s^2 + s + 2}{s} \right) - sI_0$$

$$\text{and, } 2I_1 = -sI_1 + (s+2)I_0$$

$$\text{or, } 0 = -I_1(s+2) + I_0(s+2)$$

$$\Leftarrow \text{yields } I_1 = I_0$$

$$V_I = I_0 \left[\frac{s^2 + s + 2 - s^2}{s} \right]$$

$$I_0 = \frac{V_I(s)}{s+2}$$

$$\text{In steady state, } V_I = 4\angle 0^\circ \text{ V } s \rightarrow j\omega$$

$$I_0 = \frac{4\angle 0^\circ (j2)}{2+j2} = 2\sqrt{2} \angle 45^\circ \text{ A}$$

$$i_o(t) = 2\sqrt{2} \cos(2t + 45^\circ) \text{ A}$$